

Advanced Power System Analysis (EE-908)

Time: 3 hours

Full Marks: 70

- (i) Answer any three questions from Group -A and any two from Group -B
- (ii) Marks are indicated in the margin
- (iii) The symbols are of usual meanings

GROUP - A

- 1.(a) What are the (i) loops and basic loops, and (ii) cut-sets and basic cut-sets?
- (b) With reference to Figure 1, show basic loops and basic cut-sets.
- (c) Draw and define primitive networks in impedance and admittance forms for 1- ϕ network. (4+6+4)

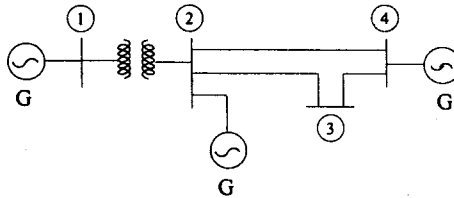


Figure 1: Problem 1(b)

- 2.(a) Establish the relationship $Z_{BUS} = (A^t [y] A)^{-1}$.
- (b) The pu reactances of the elements of Figure 2 are shown with the network diagram. The circled numbers indicate bus numbers and the underlined numbers indicate transmission line numbers. Assuming bus ① as reference and neglecting mutual couplings, compute Y_{BUS} using $Y_{BUS} = A^t [y] A$. (7+7)

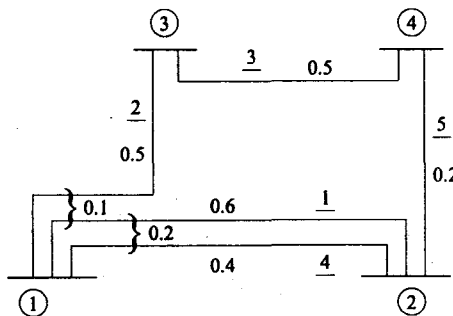


Figure 2: Problems 2(b) & 3

3. The following symmetric elements of bus impedance matrix is obtained after connecting an element 6 between bus ④ and bus ② in Figure 2 which has self reactance of 0.3 pu and is coupled to element 5 with mutual reactance of 0.1 pu.

$$Z_{22} = 0.2697 ; Z_{23} = 0.1285 = Z_{32} ; Z_{24} = 0.2344 = Z_{42} ; Z_{33} = 0.3403 ;$$

$$Z_{34} = 0.1816 = Z_{43} ; Z_{44} = 0.3462$$

Also given that the inversion of

0.2	0.1
0.1	0.3

 is

6	-2
-2	4

.

Modify the above bus impedance elements after removing the element 6 from the network. (14)

- 4.(a) (i) Why is short circuit studies needed? (ii) What are the assumptions made in representing a power system network for short circuit studies?
- (b) In admittance form of representation of fault circuit, derive general expressions for (i) current at the faulted bus; (ii) voltage at the faulted bus; (iii) voltages at the buses other than the faulted bus and (iv) fault currents flowing through the elements in phase components. ((2+2)+(4+1+1+4))

GROUP - B

5. In an existing n bus power system, a phase shifting transformer with a complex ratio $a_s + jb_s$ is being newly connected between two existing buses \textcircled{P} and \textcircled{Q} . Explain in detail how different elements of existing bus admittance matrix will get changed. Derive any mathematical expression used for this purpose. (14)
6. Justify the following:
- (i) Choice of slack bus is a must in load flow study
- (ii) $P - \delta$ and $Q - |V|$ couplings are strong but $P - |V|$ and $Q - \delta$ couplings are weak
- (iii) On-line load flow studies are time critical
- (iv) D.C. load flow method is not an iterative method and it does not provide any information on Q-flows through lines or voltage magnitudes at buses (3+4+3+4)
7. State the assumption made in Fast Decoupling Load Flow (FDLF) method, derive the voltage the voltage equations and describe the FDLF algorithm. (14)