

Advanced Instrumentation (ETC-1014)

Time: 3 hours

Full marks: 70


Answer any five questions

- 1.a. Design a scheme to measure a wide dynamic range of resistance from $1M\Omega$ to $10k\Omega$ with a resolution of 0.1% in the entire range.
b. Design an instrumentation scheme to measure both the capacitance and resistance of a sensor whose resistance is within $10k\Omega$ to $100k\Omega$ and the frequency independent capacitance is between $10nF$ to $100nF$.
(7+7)
2. Design a portable signal conditioning unit to measure the response of an impedance sensor whose sensitivity varies with frequency. The specifications are:
i) Amplitude of applied sine wave: $<100mV$
ii) Frequency of operation— $100Hz$, $300Hz$, $1kHz$, $5kHz$.
iii) Impedance of sensor resistance varies from $1k\Omega$ to $10k\Omega$
iv) Maximum sensitivity has to be displayed on LCD.
(14)
- 3.a. Why MOS transistors are used in the design of ASIC chips?
b. Obtain the small signal voltage gain for the following:
i) Constant current source load common source MOS amplifier.
ii) Diode connected load common source MOS amplifier
(4+10)
- 4.a. Draw the circuit of a cascode amplifier and obtain its small signal gain. Explain the origin of the gain.
b. Indicate the various capacitances associated with a MOS transistor and obtain the bandwidth of a common source, common drain and a common gate amplifier.
(7+7)
- 5.a. Obtain the small signal voltage gain of a double ended differential amplifier.
b. Plot the dc transfer characteristics showing the variation of current and output voltage with input common mode voltage.
(7+7)
6. What is CMRR? Obtain the expression of CMRR in a double ended differential amplifier if (i) there is a mismatch between the load resistors and (ii) if there is a mismatch in the transconductance values of the MOS transistors.
(14)

- 7.a. Explain the reason for a high voltage gain in a single ended differential amplifier.
 b. Obtain the small signal voltage gain of a single ended differential amplifier.

(7+7)

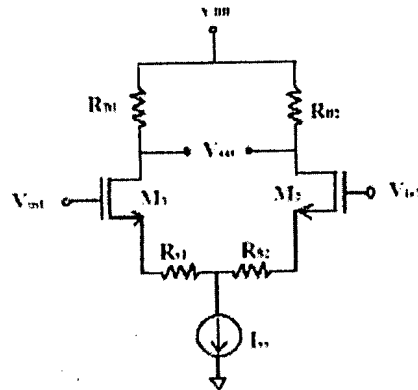8. Assuming no symmetry, calculate the small signal voltage gain in Fig.1.



(14)

Fig.1
