

**M.E. (ETC) 1<sup>st</sup> Semester Examination, 2011**  
**Active Network Analysis and Synthesis (ETC-919)**

Time: 3 hours

Full Marks: 70

*Answer question number 6 and any three questions from the rest.*

- (1) (a) Write down the properties of Network Functions. Check whether the function  $H(s) = s/(s^2 - 3s + 4)$  is stable or not?
- (b) Write down the special properties of passive RC driving point impedance function. How such functions can be written in partial fraction expansion form? Synthesis the DP function  $Z(s) = (s+2)/(s^2 + 4s + 3)$
- (c) Sketch the approximate magnitude and phase plot of a transfer function:  $H(s) = s^2 + as + b$ . Derive the expression of pole frequency and pole-Q in term of a and b. How do the magnitude and phase vary with frequency?
- (5+6+6)
- (2) (a) Write down the characteristics of Butterworth approximation function. Derive the expression of loss function in term of normalized frequency.
- (b) Find the loss at stopband edge frequency 45 rad/sec for a 3th order Butterworth filter that has a maximum loss 0.5 dB at the pass band edge frequency of 9 rad/sec Draw the delay characteristics of the function.
- (c) For Butterworth approximation function, prove that its 2n numbers of roots are located on the unit circle and are equally spaced at  $\pi/n$  radian intervals. Hence find out the approximate function for the 3<sup>rd</sup> order normalized Butterworth lowpass filter.
- (6+5+6)
- (3) (a) Draw the positive feedback biquad topology. Analyzing the feedback and feedforward transfer functions, find out the overall transfer function. Explain the special properties for such topology.
- (b) Find out the transfer function of the active circuit given in Figure-1. Obtain the expressions for filter parameters using coefficient-matching technique.

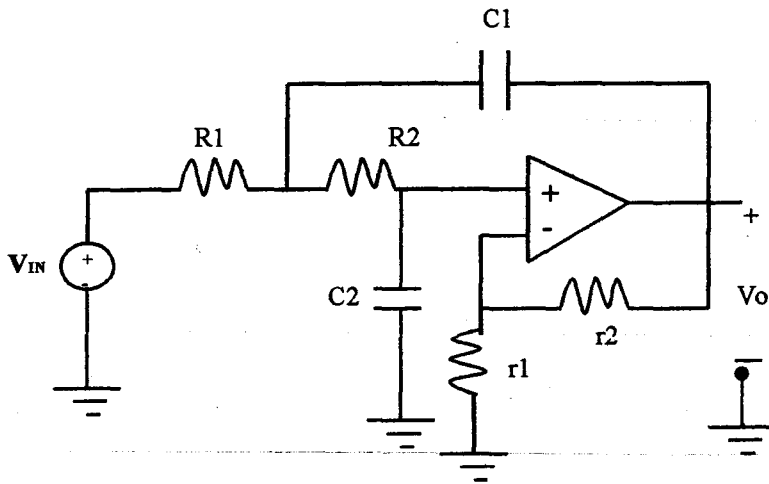


Figure-1

(c) Find out the sensitivity terms of the different parameters of the filter function.

(6+6+5)

(4) (a) How do you realized a lowpass filter function  $T(s) = -d / (s^2 + as + b)$  using three amplifier?

(b) How do you realize a general biquadratic function using an addition amplifier to the earlier circuit?

(9+8)

(5) (a) What do you understand by low sensitivity of passive network?

(b) Write down the different steps for synthesis the network function of a singly terminated ladder network

(c) Explain Zero shifting technique in this context.

(3+8+6)

(6) Write short notes (any two)

(9.5 x 2)

(a) Delay Equalizer

(b) GYRATOR

(c) Switched capacitor network

(d) FDNR