

BENGAL ENGINEERING AND SCIENCE UNIVERSITY, SHIBPUR
B.E.(EE) 3rd Semester Final Examination 2012

Subject: Network Theory

Paper / Code No: EE – 301
Time: 3 HRS.

Branch: Electrical Engineering
Full Marks: 70

- i) Answer any SIX questions taking THREE from each half.
- ii) TWO marks are reserved for neatness in each half

FIRST HALF

- 1. (a) State and prove the Compensation Theorem for AC networks.
- (b) In the circuit of Fig.1 find the current through the 5Ω resistor using principle of superposition.

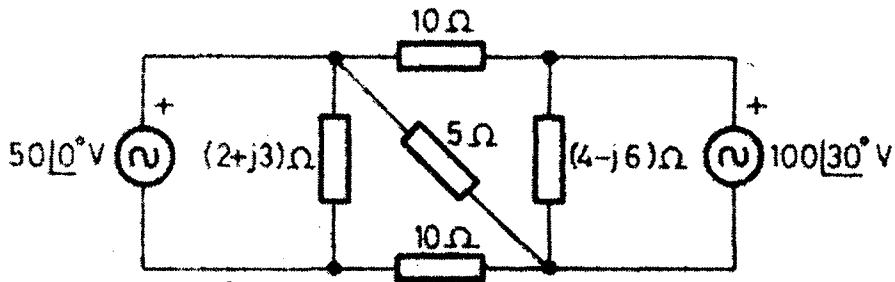


Fig.1

[5+6]

- 2. (a) State and verify the Tellegen's Theorem in a d.c. network.
- (b) Find Norton's Equivalent Network to the left of the terminals X and Y in Fig.1

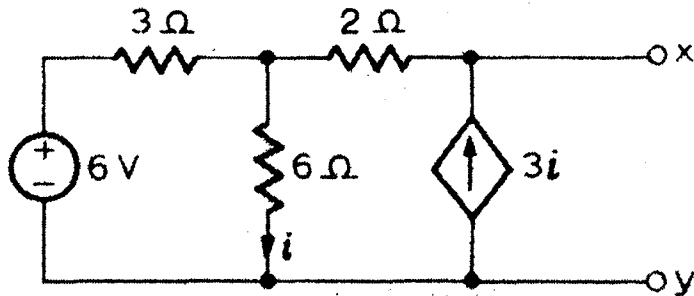


Fig.2

[5+6]

3. (a) State and prove the Maximum Power Transfer Theorem for AC networks.
 (b) In the circuit of Fig.3 find the current through Z_L using Millman's Theorem.

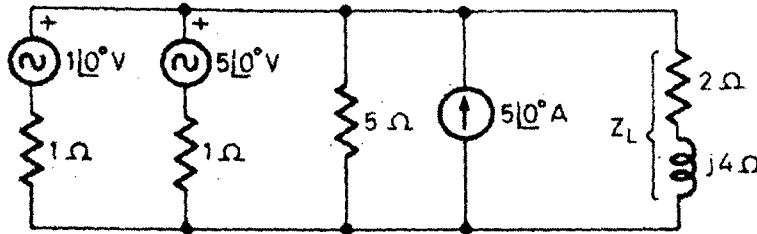


Fig. 3

[5+6]

4. (a) State and prove the Initial and Final Value Theorems in Laplace Transform.
 (b) In the circuit of Fig.4, the switch K was initially at x before $t=0$ and the circuit reached steady state. At $t=0$ the switch is shifted to y. Find the voltage across the terminals a and b for $t>0$. Assume zero initial condition for L_2 .

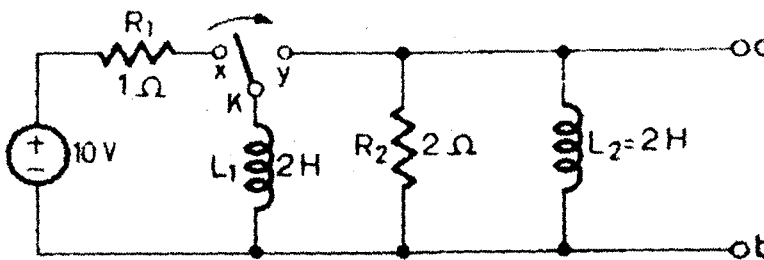


Fig.4

[5+6]

5. (a) Derive the Exponential form of the Fourier series from Trigonometric form of the series.
 (b) Find the Trigonometric Fourier series of the waveform shown in Fig.5

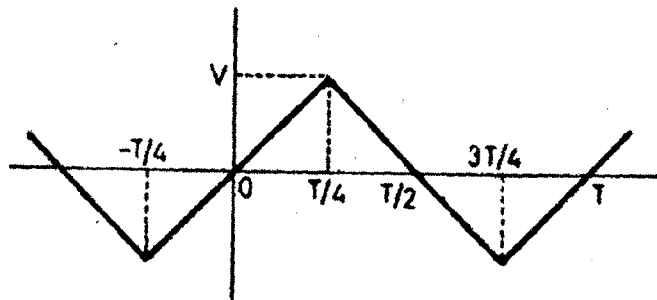


Fig. 5

[5+6]

SECOND HALF

6. a) Discuss the properties of a driving point function and a transfer function?
b) Verify whether the following functions satisfy the conditions of a valid driving point function or a valid transfer functions or both.

$$(i) N_1(s) = \frac{s^2 - s + 2}{5s^2 + 2s + 1} \quad (ii) N_2(s) = \frac{4}{s^3 + 2s} \quad (iii) N_3(s) = \frac{4s^2 + s + 7}{s + 5}$$

- c) Find the driving point impedance function for the network shown in Fig. Q-6(c). Show the poles and zeros of the network function on complex frequency plane.

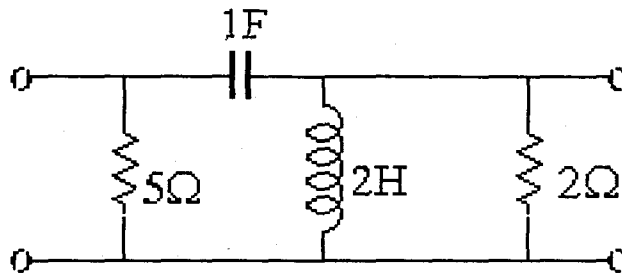


Fig. Q-6(c)

[5 + 3 + 3]

7. a) What are the transmission parameters of a network? Where are they used?
b) Find the conditions of reciprocity and symmetry of a two-port network in terms of its transmission parameters.
c) Find the suitable parameters of the network shown in figure Q-7(c) considering it as a combination of two interconnected networks.

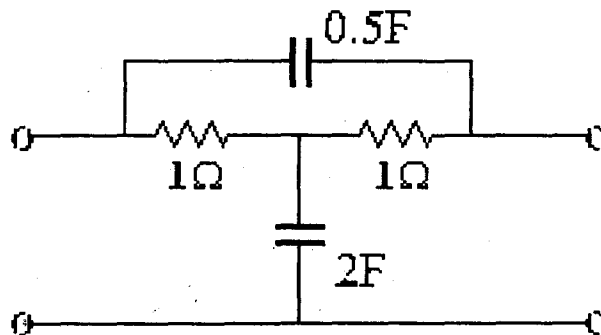


Fig. Q-7(c)

[3 + 4 + 4]

(2)

8. Write the equilibrium equations of the mechanical system shown in Fig.8. Draw the electrical analogous network for the system using $T-i/f-i$ analogy. [11]

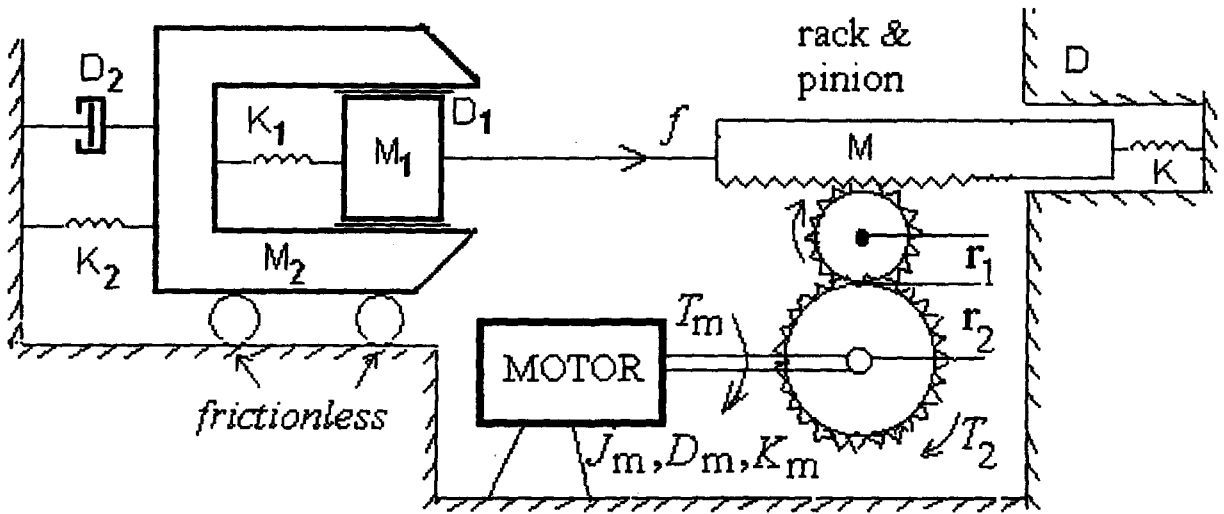


Fig. 8

9. a) Find the voltage transfer function of the network given in Fig. Q-9(a).

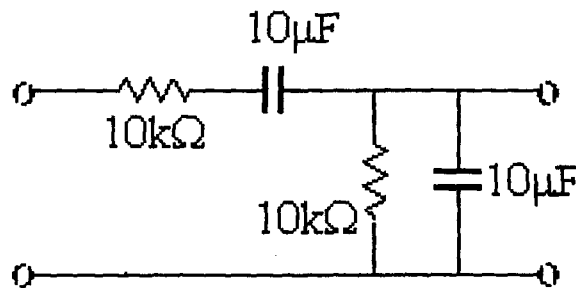


Fig. Q-9(a)

- b) Show the critical frequencies of the above network function and draw the gain-frequency plot of the output voltage response on semi-log graph paper. [3 + 8]
10. a) Explain the terms 'short-circuit impedance', 'open-circuit impedance' and 'image impedance' with respect to a two-port network. [3]
- b) Write critical notes on any two: [4x2=8]
- Electrical analogous network of water heater (thermal) system.
 - h -parameters in terms of Z -parameters.
 - Energy stored in a mutually coupled inductor.