

**Industrial Power Electronics (EE-702)**

**Time : 3 hours**

**Full Marks : 70**

Use separate answer-script for each half.  
Answer any **SIX** questions, taking **THREE** from each half.  
Two marks are reserved for neatness in each half.

---

**FIRST HALF**

1. a) The latching current of a thyristor connected in between a d.c. voltage source of 200V and the load is 50 mA. The duration of the firing pulse is 50  $\mu$ s. The load consists of a resistance of 20  $\Omega$  in series with an inductance of 0.5 H. Will the thyristor get fired? Give reasons.
- b) Explain the purpose of connecting i) a resistor across gate-cathode terminals ii) a diode in series with gate circuit and iii) a capacitor across gate-cathode terminals, of a thyristor.
- c) For a GTO,  $\alpha_1=0.3$ ,  $\alpha_2=0.85$  and  $I_A=1$  A. Find the value of turn-off gain. The symbols have their usual meanings.
- d) Explain the following ratings of an SCR and state their significances:  
(i)  $V_{DWM}$  (ii)  $V_{RSM}$

Indicate the locations of the above voltage ratings on a typical static i-v characteristic of a thyristor.

[3+3+2+3]

2. a) Explain the turn-on and turn-off processes of a GTO with the help of the two transistor analogy. Discuss the merits and demerits of a GTO as compared to a conventional thyristor.
- b) Following are the parameters and ratings of an UJT.

Inter-base voltage ( $V_{BB}$ ) = 12 V, Inter-base resistance ( $R_{BB}$ ) = 5.6 k $\Omega$

Intrinsic stand-off ratio ( $\eta$ ) = 0.63, Valley-point current ( $I_v$ ) = 4 mA

Valley-point voltage ( $V_v$ ) = 2 V, Peak-point current ( $I_p$ ) = 5  $\mu$ A

The maximum gate voltage ( $V_{GD}$ ) that will not trigger the SCR = 0.18V

Design a suitable UJT based trigger circuit for a single-phase converter (rectifier) operating from a 50 Hz ac mains supply.

[(3+3)+5]

3. a) The specified limits for  $di/dt$  and  $dv/dt$  for an SCR are  $60 \text{ A}/\mu\text{s}$  and  $300 \text{ V}/\mu\text{s}$  respectively. The supply voltage is  $240 \text{ V d.c.}$  Determine the values of the snubber circuit parameters and the value of the inductor used to limit  $di/dt$ . Take the damping ratio as  $0.7$ . Derive the various expressions used.

b) Explain the constructional details of an IGBT. Discuss its transfer and output characteristics.

[4+(4+3)]

4. The following data are specified for a  $415 \text{ V}$ ,  $2.2 \text{ kW}$ ,  $1450 \text{ r.p.m.}$  separately excited d.c. motor and its speed control system employing armature drop compensation:

Back emf constant =  $0.27 \text{ V/r.p.m.}$

Armature circuit resistance =  $2.2 \Omega$

Armature circuit inductance =  $0.02 \text{ H}$

Total moment of inertia of motor and load =  $2.2 \text{ kg-m}^2$

Output resistance of controlled rectifier =  $2.4 \Omega$

Filter choke inductance =  $0.1 \text{ H}$

Firing circuit and controlled rectifier combination gain =  $50$

Current transducer gain =  $75 \text{ mV/A}$

i) Calculate the gain of the summing amplifier to achieve critical damping.

ii) Calculate the percent speed regulation and hence the no-load speed.

iii) Calculate the reference input to the current comparison amplifier to limit the armature current to  $125 \%$  of the full-load value.

iv) Calculate the damping ratio of the system if the current feedback loop is opened. [3+4+2+2]

5. Write short notes on:

[3+4+4]

a) Advantages of A.C. Drives

b) Transfer and Output characteristics of Power MOSFETs

c) Schottky diode

## SECOND HALF

6. Explain the terms which are used as performance factors of a rectifier. Compare the performance factors of a single phase half-wave diode rectifier and a single phase full-wave diode bridge rectifier.

[3+8]

7. (a) What do you mean by CCM and DCM operation of a converter? Derive the expression for current through an R-L-E load connected to the output of a 3-phase full controlled rectifier under continuous conduction mode of operation.

(b) Draw the circuit diagram of a single phase semi-converter and explain the operation of this converter. Mention the merits and demerits of semi converter over full converter.

[(1+5)+5]

8. (a) Draw the circuit of a buck converter and explain its operation with the help of necessary waveforms.

(b) Design a buck converter having following specifications:

Input voltage = 100 V

Output voltage = 20 V

Switching frequency = 25 kHz

Maximum allowable ripple in output voltage = 1% of rated value

Maximum power output = 200W

Any other data, if required, should be assumed with proper justification.

[6+5]

9. (a) Explain the operation of a 3 phase bridge inverter for 180° conduction mode. Draw the phase and line voltage patterns of output voltage for a star connected balanced load and derive the expression for rms value of line voltage.

(b) Explain how output voltage of a single phase inverter can be adjusted by PWM technique.

[7+4]

10. (a) Prepare a brief write-up on flyback converter.

(b) Explain the operation of a single phase Auto-Sequentially Commutated (ASC) Current Source Inverter.

[6+5]