

B.E. (EE) 3rd Semester Final Examination 2011

Subject: Network Theory

Paper / Code No: EE – 301

Branch: Electrical Engineering

Time: 3 Hrs.

Full Marks: 70

- i) Answer any SIX questions taking THREE from each half.
- ii) TWO marks are reserved for neatness in each half

FIRST HALF

- 1. (a) State and prove the Millman's Theorem.
- (b) In the circuit of Fig.1 find the current through Z_L using Millman's Theorem.

[5+6]

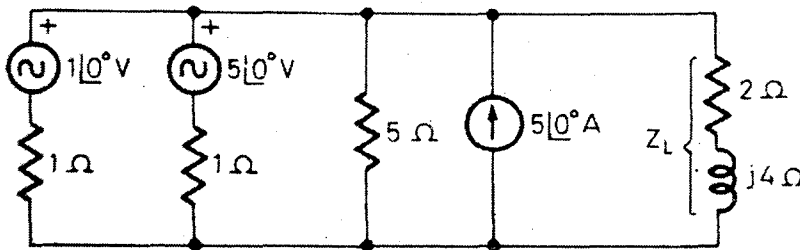


Fig. 1

- 2. (a) State and prove the Compensation Theorem for AC networks.
- (b) In the circuit of Fig.2, a $0.5\ \Omega$ resistor is added in series with the existing $1\ \Omega$ resistor. Using Compensation Theorem, determine the change in current through $1\ \Omega$ resistor after adding the new resistor,

[5+6]

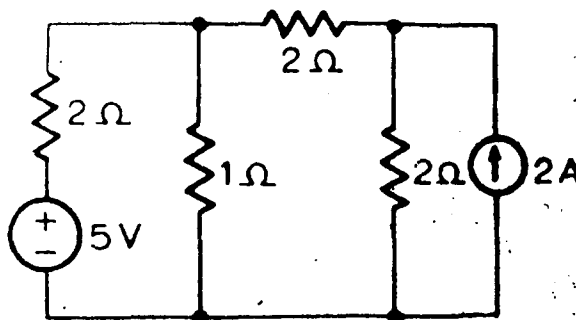


Fig. 2

3. (a) State and prove the Maximum Power Transfer Theorem for AC networks.
 (b) Find the current through the resistor R_L in Fig.3 using Norton's Theorem.

[5+6]

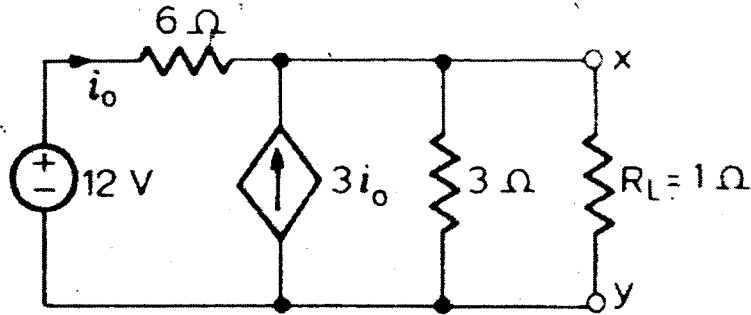


Fig. 3

4. (a) State and prove the Time Shift Theorem in Laplace Transform.
 (b) Prove that impulse function is the first order derivative of a unit step function and hence obtain the Laplace Transform of a time-shifted impulse function: $\delta(t - t_0)$

[5+6]

5. (a) Derive the Exponential form of the Fourier series from Trigonometric form of the series.
 (b) Obtain the Trigonometric Fourier series of the waveform shown in Fig.4

[5+6]

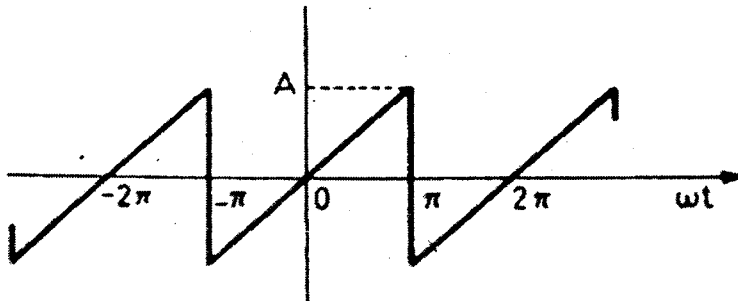


Fig. 4

SECOND HALF

6. a) Find the current transfer function $\alpha_{21}(s)$ for the network shown in Fig. 6. Find the poles and zeros of the network function and plot them on s-plane.

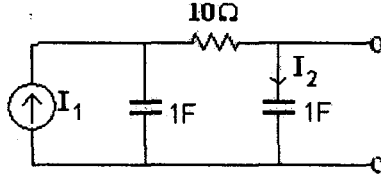


Fig. 6

- b) Draw the gain-frequency plot of the output current response on semilog graph paper.
 c) Verify whether the following satisfies the conditions of valid driving point function or valid transfer functions or both.

$$(i) N_1(s) = \frac{s^2 + s + 2}{3s^2 + 2s + 1} \quad (ii) N_2(s) = \frac{4}{s^3 + 2s}$$

[3 + 6 + 2]

7. a) Find the short circuit parameters of the network shown in Fig.-7(a)

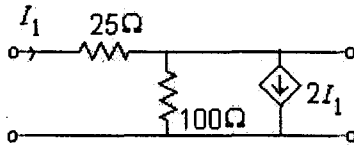


Fig. 7(a)

- b) Determine the transmission parameters of the network shown in Fig. 7(b) considering two identical sections connected in cascade manner.

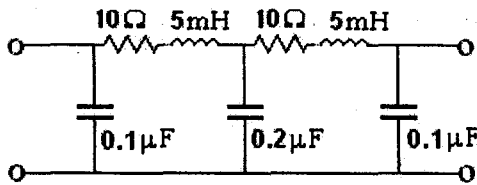


Fig. 7(b)

- c) Establish the conditions of reciprocity and symmetry for the g-parameters.

[4 + 4 + 3]

8. Write the equilibrium equations of the mechanical system shown in Fig.8. Draw the electrical analogous network for the system using $T-i/f-i$ analogy. [11]

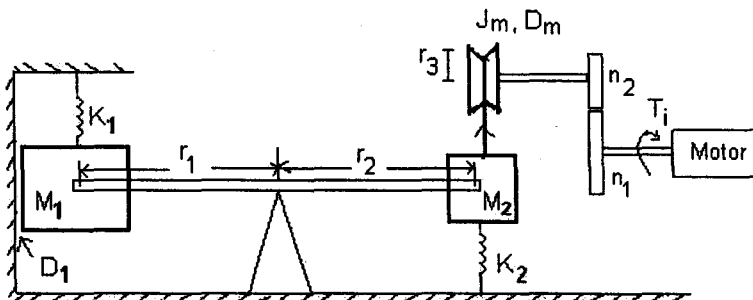


Fig. 8

9. a) Find the energy stored in two mutually coupled inductors and hence determine the maximum possible value of the mutual inductance in terms of the self inductances of the coils.
- b) Find the voltage across 5Ω resistance in the magnetically coupled network shown in Fig. 9(b).

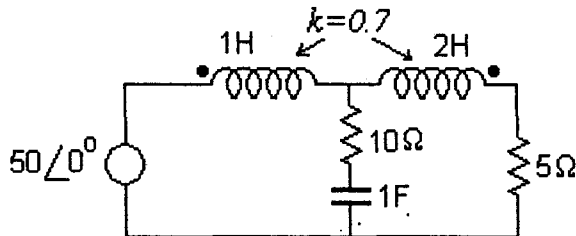


Fig. 9(b)

- c) Calculate the equivalent inductance of three mutually coupled inductors connected in series as shown in Fig. 9(c).

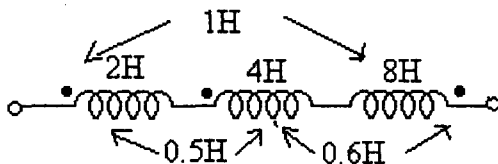


Fig. 9(c)

[4 + 4 + 3]

10. Write short notes on (any two)

[5½ x 2]

- i) Electrical analogous network of two tank liquid level system.
- ii) T-parameters in terms of h-parameters
- iii) Necessary conditions of a Transfer Function
- iv) Effect of poles and zeros on time domain response