

Time: 3 hours

Full marks: 70

Part-A

(Answer question number 1 and any One from the rest)

1. (a) Explain with examples, different types of logic hazards? How to minimize them?
 (b) Design an additive array multiply module to implement following function

$$P = AXB + C + D$$

$$(A = a_3 a_2 a_1 a_0, B = b_1 b_0, C = c_3 c_2 c_1 c_0, D = d_1 d_0)$$
(15)

2. (a) Write down the CORDIC algorithm for both vectoring and rotation operation. Perform VLSI design for a pipelined CORDIC processor for both operations. Explain also the various sub-blocks used in this design.
 (b) Explain with circuit diagram the operation of Four bit parallel unsigned binary divider.
 (20)


3. (a) Write down the decimation-in-frequency FFT algorithm with 8 point signal flow graph. Describe the address generation block for the abovementioned algorithm.
 (b) Design a arbitrary counter using D flip flops which will generate the sequence 2, 9, 7, 11, 5, 8 and repeats thereafter.
 (20)

Part-B


(Answer question number 5 and any two from the rest)

4. [Choose the correct alternative]
 - a) Threshold voltage (V_t) of MOSFET
 - i) Increases with increased doping and decreases with decreased oxide thickness
 - ii) Increases with increased doping and increases with decreased oxide thickness
 - iii) Decreases with increased doping and decreases with decreased oxide thickness
 - iv) Decreases with increased doping and increases with decreased oxide thickness

 - b)

 

 For body bias effect input and output voltage relation is like



- c) In saturation region of a MOS
- Static resistance is high, dynamic resistance is low
 - Static resistance is low, dynamic resistance is high
 - Static resistance is high, dynamic resistance is high
 - Static resistance is low, dynamic resistance is low
- d) Switching Threshold voltage of CMOS inverter
- Increases
 - Decreases
 - First decreases then increases
 - remain unchanged with increasing transconductance ratio (k_n/k_p).
- e) If initial doping density is N_A then after constant voltage scaling it becomes (S =scaling factor)
- SN_A
 - S^2N_A
 - S^3N_A
 - Remain same.


1x5=5

5. a) Amongst a CMOS NAND and NOR gate which one is better and why?
 b) Discuss the factors on which threshold voltage of MOS transistor depends.
 c) Derive the expression for switching threshold voltage of the CMOS NOR2 gate


4+5+6=15

6. a) Discuss the operation of the circuits shown below and find 'f'.

i)

 

ii)

 

- b) What is the problem of pass transistor logic and how that problem can be solved?

9+6=15

7. a) Discuss various voltage dependent capacitances of MOSFETs. In which region (s) MOS offers the maximum capacitance and why?
 b) How the linearity of the switch capacitor circuit can be improved?

8+7=15