

**NETWORK THEORY**  
**(ET-302)**

Time : 3 Hours

Full Marks : 70

**Answer Question no.1 and any FOUR from the rest**  
**(Extra Answers will be discarded)**

1. Pick up the correct answer(s) (any Six). 1×6=6
- (a) The number of loop equations required to completely analyze a network comprising nine independent branches and five nodes including the reference node shall be  
(i) 5                      (ii) 4                      (iii) 3                      (iv) 6
- (b) The impedance of a capacitive reactance varies  
(i) linearly with frequency                      (ii) hyperbolically with frequency  
(iii) parabolically with frequency                      (iv) exponentially with frequency                      (v) none of these
- (c) Power dissipated in a pure capacitor is  
(i) zero                      (ii) maximum                      (iii) minimum                      (iv) none of these
- d) The product  $RC$  has dimension of  
(i) ohm                      (ii) farad                      (iii) second                      (iv) herz
- (e) Bandwidth ( $\Delta f$ ) of a series resonant circuit is given be  
(i)  $\frac{R}{L}$                       (ii)  $\frac{Q_0}{f_0}$                       (iii)  $\frac{R}{4\pi L}$                       (iv)  $\frac{R}{2\pi L}$
- (f) Condition for reciprocity of network (pick up wrong relation)  
(i)  $z_{12} = z_{21}$                       (ii)  $y_{12} = y_{21}$                       (iii)  $h_{12} = -h_{21}$                       (iv)  $AD + BC = 1$
- (g) Branches removed from a graph in forming a tree are called  
(i) links                      (ii) cotree                      (iii) twigs                      (iv) chords
- (h) Laplace transform of 't' is  
(i) 1                      (ii) s                      (iii) 1 / s                      (iv) 1 / s<sup>2</sup>
2. (a) Define poles and zeros of a network function. Draw the pole-zero diagram of the network function  $N(s) = \frac{(s+1)^2(s+5)}{(s+2)(s^2+6s+13)}$
- (b) The driving point impedance of a one-port network is given by  $Z(s) = \frac{2s(s^2+2)(s^2+4)}{(s^2+1)(s^2+3)}$   
Determine the first Foster form of the network showing all the calculations in details.
- (c) The driving point impedance of a network is given by  $Z(s) = \frac{(s+2)(s+4)}{s+3}$   
By inspection find the type and number of elements in the synthesis of the network for the above function. State the criteria that you have used here in reaching your results.

4+9+3=16

3. (a) Derive the condition for maximum power transfer from a source to a load when the load resistance and reactance are varied independently. Show all the detailed steps of derivative while deriving. From the condition write the statement of maximum power transfer to a load.
- (b) For the circuit shown in Fig.3(b), what load impedance  $Z_L$  absorbs maximum average power and what is this power?

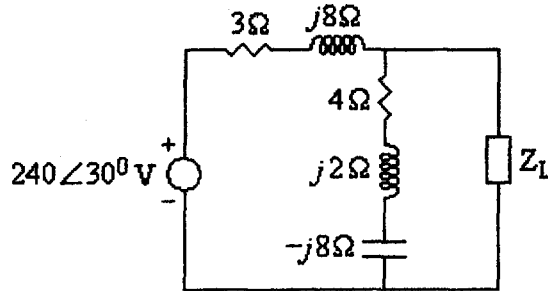


Fig.3(b)

9+7=16

4. (a) Derive with necessary diagrams the equivalence between a voltage source  $V_S$  with series impedance  $Z_V$  and a current source  $I_S$  in parallel with impedance  $Z_I$ .
- (b) With suitable diagrams explain voltage source shifting technique. In which kind of circuit configuration is this method used conveniently?
- (c) Find the equivalent voltage generator and current generator separately across the terminals  $A$  and  $B$  for the network given in Fig.4(c). Estimate the current in each case that would flow if a load of  $5\ \Omega$  is connected across the terminals  $A$  and  $B$  of the network. Show all the calculations and necessary diagrams.

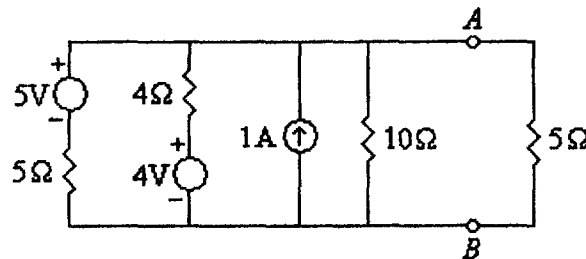


Fig.4(c)

5+5+6=16

5. (a) A pulse voltage of magnitude 10 volts and extending from 0 to 2 sec is applied at time  $t = 0$  to a series  $R$ - $L$  circuit consisting of resistance  $R = 4\ \Omega$  and inductor  $L = 2$  Henry. Assume zero current through the inductor  $L$  before application of the voltage pulse. By using Laplace transformation find current  $i(t)$ , voltages  $v_R(t)$  and  $v_L(t)$ . Neatly plot each of them superimposing with the pulse. Show the construction of  $i(t)$  waveform by drawing individual waveforms of all the terms of itself.
- (b) When a load impedance  $Z_L$  is connected across port-2 of a two-port network, find the expression for the input impedance in terms of  $z$ -parameters and the load impedance. From this show that when  $Z_L = \infty$ , the input impedance =  $z_{11}$  and for  $Z_L = 0$ , the input impedance =  $1/y_{11}$ .

11+5=16

6. (a) Draw a series  $RLC$  resonant circuit. Define its bandwidth (BW). Why is it also called 3-dB BW and half-power BW? Explain with the help of its response curve and necessary calculations. Derive that for a series  $RLC$  circuit the bandwidth is given by  $\Delta\omega = R/L$

- (b) Write the formula of the Laplace transform of any function that repeats itself. Fig.6(b) shows a square wave  $v(t)$  of amplitude unity and periodic time  $2a$ . Derive (i) without using that formula and (ii) using that formula that its Laplace transform is  $F(s) = \frac{1}{s} \frac{1 - e^{-as}}{1 + e^{-as}}$

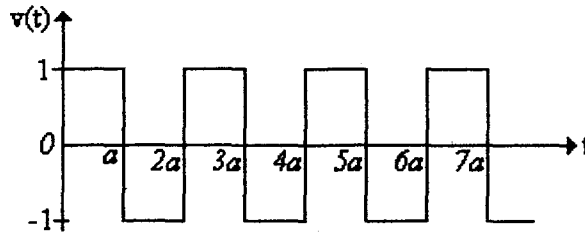


Fig.6(b)

10+6=16

7. (a) Define h-parameters. Find the y-parameters (from the definition) for the given resistive network of Fig.7(a) containing a controlled voltage.

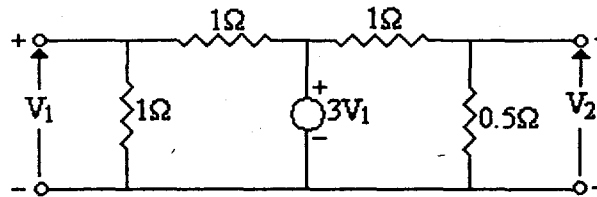


Fig.7(a)

- (b) For the circuit shown in Fig.7(b), find the complete expression for the current when the switch K is closed at  $t = 0$ .

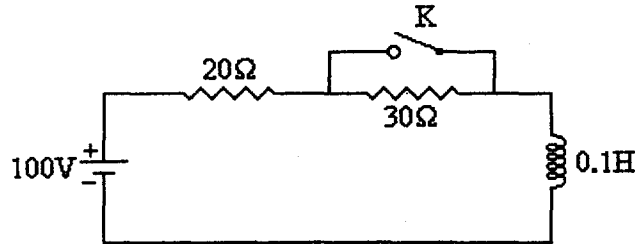


Fig.7(b)

11+5=16

8. (a) Define the terms: (i) Graph, (ii) Tree.  
 (b) For the given resistive network [Fig.8(b)] draw a graph and 12 trees. Select a tree and write a tie-set schedule and equilibrium equations on the current basis. Solve these equations and calculate the branch currents and branch voltages. Given that  $R_1=5\Omega$ ,  $R_2=5\Omega$ ,  $R_3=R_4=R_6=10\Omega$  and  $R_5=2\Omega$ .

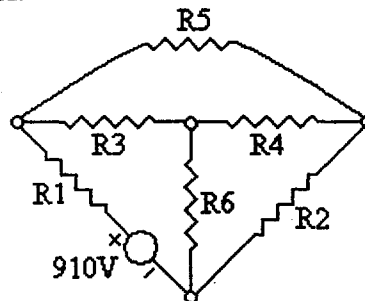


Fig.8(b)

3+13=16