

Answer any five questions.

Answer should be brief and to the point.

Unnecessary lengthy answers may result in loss of marks.

- Explain reverse recovery characteristics of power diode
 - The reverse recovery time of a diode is $t_{rr} = 5 \mu s$ and the rate of fall of diode current is $di/dt = 80 A/\mu s$. If the softness factor is $SF = 0.5$, determine (i) the storage charge Q_{rr} , and (ii) the peak reverse current. (7+4+3)
- Draw v-i characteristic of SCR and explain it. Draw two transistor equivalent circuit of Thyristor and explain how on state is achieved.
 - How thyristor can be protected against di/dt and dv/dt triggering? (2+6+6)
- The bipolar transistor in fig- 1. is specified to have β_F in the range of 10 to 40. The load resistance is $R_C = 11 \Omega$. The dc supply voltage is $V_{CC} = 200 V$ and the input to the base circuit is $V_B = 10 V$. If $V_{CE(sat)} = 1.0 V$ and $V_{BE(sat)} = 1.5 V$, find (a) the value of R_B that results in saturation with an ODF(Over Drive Factor) of 5 (b) β_{forced} , and (c) the power loss P_T in the transistor. Deduce any formula you use. (5+4+5)

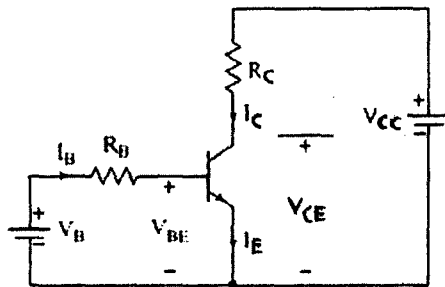


Fig - 1

- Draw the schematic construction of a vertical MOSFET. Draw its parasitic model and explain its operation. (6+8)

5. (i) If the rectifier in Fig - 2 has a purely resistive load of R , determine (a) the efficiency, (b) the FF, (c) the RF, (d) the TUF.
 (ii) Find the Fourier Series of the output voltage of the rectifier (8+ 6)

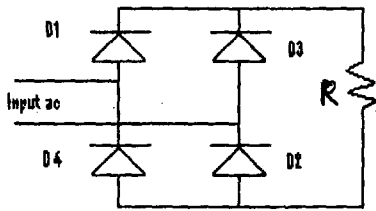


Fig - 2

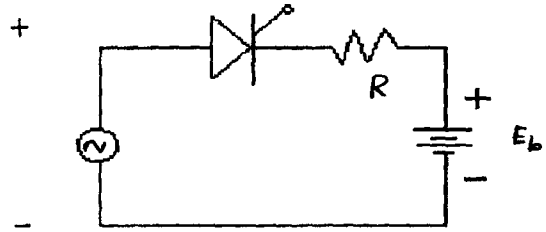


Fig - 3

6. (i) What are the problems of series connected diodes, and what are the possible solutions?
 (ii) Two diodes are connected in series to share a total dc reverse voltage of $V_D = 5$ KV. The reverse leakage current of the two diodes are $I_{s1} = 30$ mA and $I_{s2} = 35$ mA. (a) Find the diode voltages if the voltages-sharing resistances are equal, $R_1 = R_2 = R = 100$ k Ω . (b) Find the voltages-sharing resistances R_1 and R_2 if the diode voltages are equal, $V_{D1} = V_{D2} = V_D/2$ (3+7 + 4)
7. (i) A DC battery is charged through a resistor R by a half wave thyristor controller as shown in the Fig -3. Derive an expression for the average value of charging current in terms of E_m , E_b , R etc. on the assumption that SCR is fired continuously and neglect drop across SCR.
 (ii) Find conduction angles and show on the voltage & current wave forms, charging current for 230V, 50Hz AC input, $R = 5\Omega$ and $E_b = 150$ V
 (iii) Find the power supplied to the battery and that dissipated in the resistor. (6+5+3)
8. (i) Discuss the operation of a boost regulator with the help of neat circuit diagram and waveforms assuming load current is continuous.
 (ii) A boost regulator has an input voltage $V_s = 6$ V The average output voltage, $V_a = 18$ V and average load current, $I_a = 0.4$ A The switching frequency is 20 KHz. If $L = 250$ μ H and $C = 420$ μ F, determine (a) the duty cycle k (b) the ripple current of inductor, ΔI , (c) the peak current of inductor, I_2 (d) the ripple voltage of capacitor, ΔV_c and (e) the critical value of L_c and C_c . (6+8)
9. Discuss UJT firing circuit with the help of a circuit diagram and its characteristics. An UJT oscillator circuit having following parameters: $V_s = 30$ V, $\eta = 0.51$, $I_p = 10\mu$ A, $V_v = 3.5$ V, $I_v = 10$ mA, $R_{b1} = 100$ ohm, $R_{b2} = 654$ ohm, $R = 46.7$ Ω , $C = 0.5\mu$ F, width of pulse is $t_g = 50$ mS, assume $V_d = 0.5$ V(may be neglected if necessary). Find the operating frequency. How triggering circuit can be isolated from power circuit? (10+4)