

**B.E (ETC) 7<sup>th</sup> Semester Final Examination, 2013**  
**Subject: VLSI Logic Design (ET 706/3)**

**Time: 3 hours**

**Full marks: 70**

**Use separate Answer script for each half**

**First Half**

**Attempt ALL questions**


1. Write down the CORDIC algorithm for both vectoring and rotation operation. Perform VLSI design for a serial CORDIC processor for both operations. Explain also the various sub-blocks used in this design. (10)
2. Write notes on
  - (i) Four bit parallel unsigned binary divider
  - (ii) Built in self test in VLSI(10)
3. (a) Explain with the help of flow chart the various steps in VLSI design flow.  
(b) Design an additive array multiply module to implement following function  
 $P = AXB + C + D$   
( $A = a_3 a_2 a_1 a_0$ ,  $B = b_1 b_0$ ,  $C = c_3 c_2 c_1 c_0$ ,  $D = d_1 d_0$ ) (15)

**Second Half**

**Attempt ALL questions**

4. Choose the correct alternative
  - A) Threshold voltage ( $V_t$ ) of MOSFET
    - i) Increases with increased doping and decreases with decreased oxide thickness
    - ii) Increases with increased doping and increases with decreased oxide thickness
    - iii) Decreases with increased doping and decreases with decreased oxide thickness
    - iv) Decreases with increased doping and increases with decreased oxide thickness

B) Assume  $V_T = 1V$

 

- i) 2V ii) 1V iii) 3V iv) 4V


C) In constant voltage scaling

- i) Power dissipation increases and power density decreases
- ii) Power dissipation decreases and power density increases
- iii) Power dissipation decreases and power density remain same
- iv) Power dissipation remain same and power density decreases

D) Threshold voltage ( $V_t$ ) of MOSFET

- i) Decreases for short channel effects and increases for narrow channel effects
- ii) Increases for short channel effects and decreases for narrow channel effects
- iii) Decreases for short channel effects and decreases for narrow channel effects
- iv) Increases for short channel effects and increases for narrow channel effects

E) For a CMOS Inverter

 

i)  $K_{R1}=4.0, K_{R2}=1.0, K_{R3}=0.25$

ii)  $K_{R1}=1.0, K_{R2}=0.25, K_{R3}=4.0$

iii)  $K_{R1}=0.25, K_{R2}=1.0, K_{R3}=4.0$  : Where  $K_R=K_n/K_p$

5x1=5

5. a) Amongst a CMOS NAND and NOR gate which one is better and why?

b) Discuss the voltage transfer characteristics of CMOS inverter with emphasis on region of operation of n-MOS and p-MOS.

c) What is the advantage of transmission gate logic over pass transistor logic?

5x3=15

6. a) What is drain induced barrier lowering?

b) How the problem of conventional dynamic circuit is circumvented by Domino logic?

c) Discuss the purpose of weak pull up transistors in Domino CMOS logic

5X3=15