

IT305: Digital Circuits and Logic Design

Answer Question No. 1 and any FIVE from the rest

FM – 70


Duration: 3 hr

1. Answer the following: 10 × 2
 - a. Perform the binary addition: $11000.11 + 101.111$. Also carry out the equivalent decimal addition.
 - b. Perform the subtraction with the following binary numbers by 2's complement method. Check the answer by straight subtraction.
 $100 - 110000$
 - c. Convert the following to the other canonical form:
 $F(x, y, z) = \Sigma(0, 2, 4, 6)$
 - d. The Boolean expressions of the two variables X and Y in terms of the three inputs A, B and C are given by

$$X = ABC + \bar{A}BC + A\bar{B}C$$

$$Y = (\bar{A} + \bar{B} + \bar{C})(\bar{A} + B + C)(A + \bar{B} + C)$$
 What is the relationship between X and Y?
 - e. An equality detector gives the output $Y = 1$ if both the inputs A and B are either 0 or 1. Construct the truth table and write the Boolean expression for Y.
 - f. Show how to implement AND with OR and NOT gates?
 - g. Show that the dual of the exclusive-OR is equal to its complement.
 - h. Show that a positive-logic AND gate is a negative-logic OR gate, and vice versa.
 - i. Give the truth table of 3-input XNOR gate.
 - j. Simplify the Boolean function (using K-map): $f(x, y, z) = \Sigma(0, 3, 5, 7)$

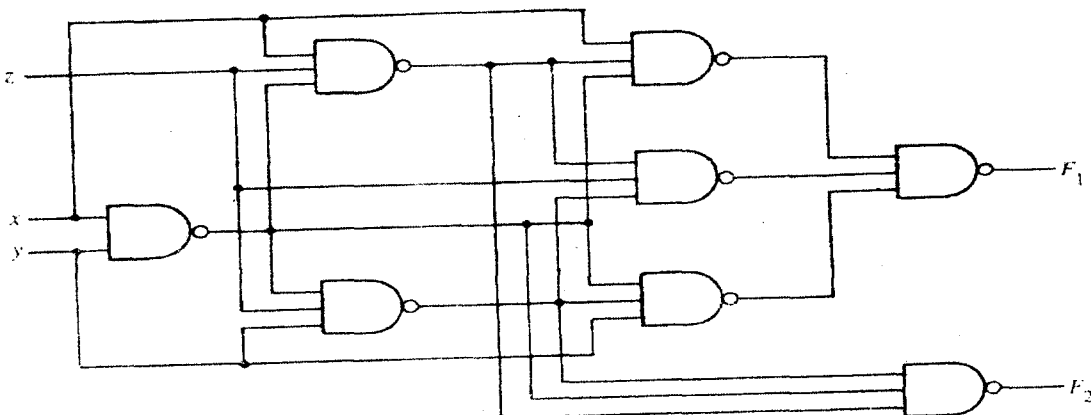2. Determine the output Boolean functions of the circuit in the following figure:



Obtain the truth table for the above circuit.

Obtain the equivalent AND-OR logic diagram of the above figure.

3 + 3 + 4

3. Design a combinational circuit that compares two 4-bit numbers, A and B, to check if they are equal. The circuit has one output x, so that $x = 1$ if $A = B$, and $x = 0$ if $A \neq B$. Clearly depict the diagram and explain its operation.

5 + 5

4. a) A combinational circuit is defined by the following two functions:

$$F_1(x, y) = \Sigma(1, 3)$$

$$F_2(x, y) = \Sigma(0, 2, 3)$$

Implement the combinational circuit by means of the decoder and external NAND gates.

b) Construct a 5×32 decoder with four 3×8 decoders and a 2×4 decoder. Use a block diagram construction.

5 + 5

5. A burglar alarm should activate when the two conditions given below are simultaneously satisfied:

a) The main entrance door of the building is open, and

b) The bedroom door and / or the kitchen door is open.

Write the truth table and construct the logic circuit to operate the alarm using one AND gate and one OR gate.

4 + 6

6. What is triggering? Classify different types of triggering. What type of triggering is used in conventional DDR RAM? Implement the expression for the output carry and sum of a 1 bit full adder circuit using a PLA.

1+2+1+6

7. What is race around condition in context to JK flip flop? Explain. How this problem is overcome? Explain with block diagram.

4+6

8. What are the differences between synchronous and asynchronous sequential circuits? Explain the principle of operation of a clocked SR flip flop with preset and clear inputs. Mention major applications of flip flops.

3+4+3

9. Explain the principle of operation of a 4 bit PISO register. How many clock cycles will be required to transfer an 8 bit data block to this register? Mention some merits and demerits of Ring counter and Johnson's counter.

5+1+4